

2.4

BOOLEAN

LOGIC

TOPIC WISE EXAM QUESTIONS


ANSWERS

GCSE


OCR

2023


<p>4 (a)</p>	<p>1 mark each, max 2 if not fully correct circuit.</p> <ul style="list-style-type: none"> NOT B AND gate with A / C as one direct input... ...Second AND gate with other (unused) A / C as direct input and output of previous stage as other input <p>Fully correct circuit is any of :</p> <ul style="list-style-type: none"> $Q = (A \text{ AND NOT } B) \text{ AND } C$ $Q = A \text{ AND } (\text{NOT } B \text{ AND } C)$ $Q = (A \text{ AND } C) \text{ AND NOT } B$ <p>See examples below :</p>	<p>3 (AO3 2a)</p> <p>Shapes of logic gates must be correct. NOT gate must include circle for inversion. No other gates should include circle.</p> <p>AND gates must have two different inputs, NOT gate must have one input. All gates must have one output.</p> <p>Correct system will always have NOT B and two other AND gates correctly joined.</p> <p>Accept alternative systems that produce the correct output.</p> <p>Accept (BOD) three input AND gate for BP2 and BP3 if used correctly.</p> <p>OK if inputs/outputs not joined up to A/B/C/Q as long as intention clear.</p> <p>If lines cross on diagram, give BOD.</p> <p>If (A AND C) AND NOT B drawn, allow NOT B as first input for BP3.</p>
--------------	--	---

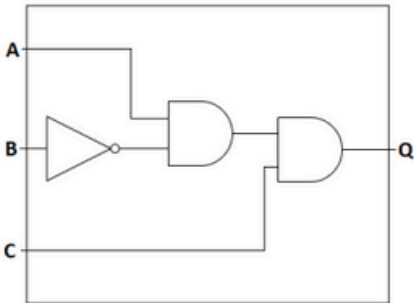

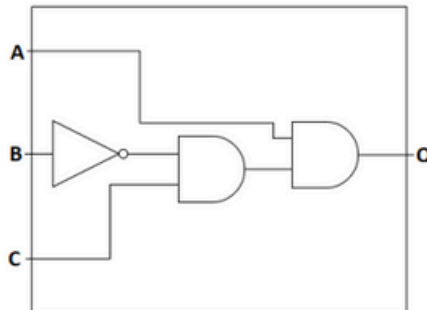$Q = (A \text{ AND NOT } B) \text{ AND } C$



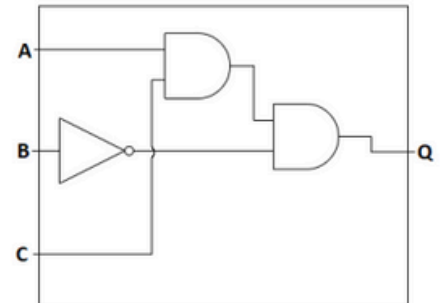
$A \text{ AND } (\text{NOT } B \text{ AND } C)$




$(A \text{ AND } C) \text{ AND NOT } B$

<p>(b)</p>	<p>1 mark each</p> <ul style="list-style-type: none"> Logic gate 1: OR Logic gate 2: AND 	<p>2 (AO2 1a)</p> <p>Allow A OR B // B OR A for logic gate 1 Allow A AND B // B AND A for logic gate 2</p> <p>If logic statement provided with multiple gates (e.g. A OR B AND C) this is incorrect.</p> <p>Allow use of symbols (e.g. \vee, $+$ for OR, \wedge, \cdot for AND)</p> <p>Allow correct drawing of logic gates.</p>
------------	--	--


2022

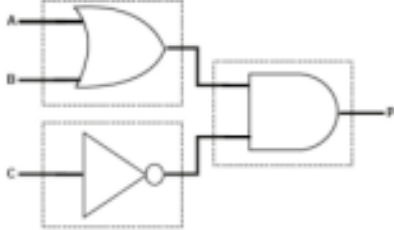2	(a)	(i)	<ul style="list-style-type: none"> A OR B NOT C AND gate 	3 (AO2 1b)	<p>1 mark per gate. Correct symbols must be used.</p> <p>NOT gate must have circle for inversion, OR and AND must <u>not</u> have a circle.</p> <p>Mark the shape of each gate, not the name written if given. Ignore any writing / notes.</p> <p>Lines do not have to be drawn or joined up, but if they are, gates must have the correct number of inputs/outputs. Penalise once then FT.</p>
2	(a)	(ii)	<ul style="list-style-type: none"> To show all possible inputs (to the logic circuit)... ...and the associated/dependent output (for each input) 	2 (AO1 1b)	<p>For 2nd BP, must be clear that the output is linked to the input values given.</p> <p>"All possible combinations of inputs and outputs" gains the first mark (all possible inputs) but not the second.</p> <p>"The output for each possible input" gains both marks</p>
2	(a)	(iii)	<ul style="list-style-type: none"> 8 // eight 	1 (AO2 1a)	Accept other answers that equate to 8 (e.g. 2 ³)

SAMPLE

1	a		<table border="1" data-bbox="191 1220 475 1355"> <thead> <tr> <th>A</th> <th>B</th> <th>P</th> </tr> </thead> <tbody> <tr> <td></td> <td></td> <td></td> </tr> <tr> <td></td> <td></td> <td>1</td> </tr> <tr> <td></td> <td></td> <td>1</td> </tr> <tr> <td></td> <td></td> <td></td> </tr> </tbody> </table>	A	B	P						1			1				2 (AO1 1b)	<p>1 mark for each correct answer in table</p> <p>'True' or 'T' are also credit worthy.</p>
A	B	P																		
		1																		
		1																		
	b			1 (AO1 1b)	Correct Answer Only															


2020

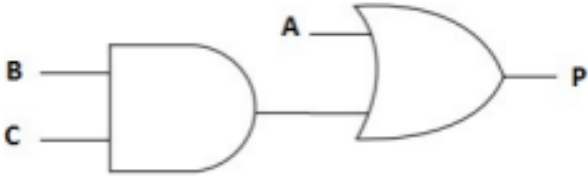4	f	i	<p>1 mark per bullet point</p> <ul style="list-style-type: none"> • B AND C • OR gate with two inputs, one of which is A • ...correct connection of these two gates with no additional gates / connections 	3	<p>Shape must be accurate</p> 															
4	f	ii	<p>1 mark per bullet point</p> <ul style="list-style-type: none"> • Correct completion of A and B inputs as 1 1 • 0 output for 01 input • 0 output for 10 input • 0 output for 11 input 	4	<p>CAO</p> <table border="1" data-bbox="997 689 1535 958"> <thead> <tr> <th>A</th> <th>B</th> <th>P</th> </tr> </thead> <tbody> <tr> <td>0</td> <td>0</td> <td>1</td> </tr> <tr> <td>0</td> <td>1</td> <td>0</td> </tr> <tr> <td>1</td> <td>0</td> <td>0</td> </tr> <tr> <td>1</td> <td>1</td> <td>0</td> </tr> </tbody> </table>	A	B	P	0	0	1	0	1	0	1	0	0	1	1	0
A	B	P																		
0	0	1																		
0	1	0																		
1	0	0																		
1	1	0																		

2019

5	(e)	<p>1 mark per missing bit</p> <table border="1" data-bbox="391 1236 1013 1585"> <thead> <tr> <th>A</th> <th>B</th> <th>Q</th> </tr> </thead> <tbody> <tr> <td>0</td> <td>0</td> <td>0</td> </tr> <tr> <td>0</td> <td>1</td> <td>1</td> </tr> <tr> <td>1</td> <td>0</td> <td>1</td> </tr> <tr> <td>1</td> <td>1</td> <td>1</td> </tr> </tbody> </table>	A	B	Q	0	0	0	0	1	1	1	0	1	1	1	1	4	<p>Accept T / True</p>
A	B	Q																	
0	0	0																	
0	1	1																	
1	0	1																	
1	1	1																	

2018

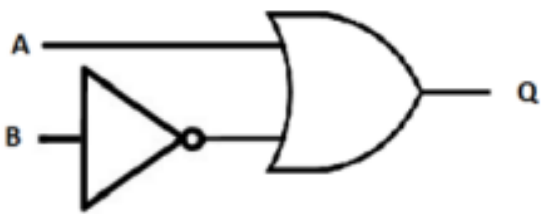3	(a)	(ii)	<table border="1" data-bbox="271 414 742 705"> <thead> <tr> <th>A</th> <th>B</th> <th>Q</th> </tr> </thead> <tbody> <tr> <td>0</td> <td>0</td> <td>1</td> </tr> <tr> <td>0</td> <td>1</td> <td>1</td> </tr> <tr> <td>1</td> <td>0</td> <td>1</td> </tr> <tr> <td>1</td> <td>1</td> <td>0</td> </tr> </tbody> </table>	A	B	Q	0	0	1	0	1	1	1	0	1	1	1	0	4	1 mark per row
A	B	Q																		
0	0	1																		
0	1	1																		
1	0	1																		
1	1	0																		
3	(b)	<p data-bbox="271 728 526 761">1 mark per bullet, max 2</p>  <ul data-bbox="271 1041 829 1124" style="list-style-type: none"> • OR gate with two inputs // NOT gate on B input • Logic system as above with no other gates, with labelled inputs of A and B. 	2	<p data-bbox="981 728 1532 817">First mark can be awarded if candidate has either a NOT gate from B, or an OR gate with two inputs anywhere in their answer.</p> <p data-bbox="981 840 1532 896">Second mark is only awarded if the logic system as shown is given with no other additional gates.</p> <p data-bbox="981 918 1532 1008">Correct logic diagrams needed for OR and NOT, including circle on NOT. Use professional judgement. Ignore labelling.</p> <p data-bbox="981 1030 1260 1064">No need to label Q output.</p>																

**If you found this
useful, drop a follow
to help me out!**

THANK YOU!

GCST